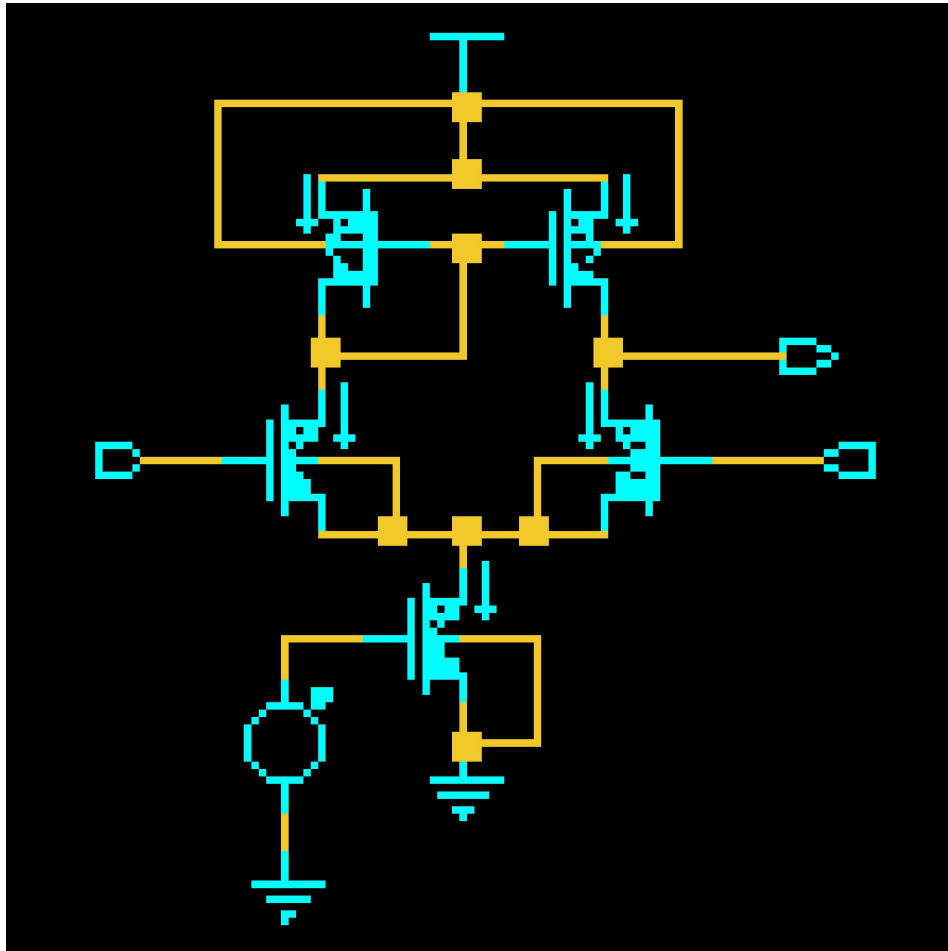


# CIRCUIT DIAGRAM

---



Differential Amplifier

## Theory:

the gain of this differential amplifier is

$$\text{Gain} = V_{\text{OUT}}/(V_1 - V_2). \text{----- (1)}$$

We can find the expression of  $V_{\text{OUT}}$  in term of  $V_1$  and  $V_2$  by using superposition theorem:

$$V_{OUT} = [R_3/(R_1+R_3)] [(R_4 + R_2)/R_2] V_1 - [R_4/R_2] V_2 \text{ ----- (2)}$$

However, we will not be able to re-arrange this expression in the form of eqn (1) to find the gain of the amplifier (except in the special case of  $R_1 = R_2$  and  $R_3 = R_4$ ).

Instead of applying superposition theorem with  $V_1$  and  $V_2$  separately, a better way is to first combined  $V_1$  and  $V_2$  in a different format, viz.  $(V_1-V_2)$ . This is known as the differential mode input -  $V_d$ . Associated with this differential mode component will be the common mode input -  $V_{cm}$ , which is equal to the average value of  $V_1$  and  $V_2$ .

$$\text{Differential mode component : } V_d = (V_1-V_2)$$

$$\text{Common mode component : } V_{cm} = (V_1+V_2)/2$$

By using these alternate representation of the input components ( $V_d$  and  $V_{cm}$ ) instead of the original components ( $V_1$  and  $V_2$ ), we can re-express eqn (2) in terms of  $V_d$  and  $V_{cm}$  as follows.

$$V_{cm} = (V_1+V_2)/2 \Rightarrow 2V_{cm} = V_1 + V_2 \text{ ---- (3)}$$

$$\text{Since } V_d = V_1 - V_2 \text{ ---- (4)}$$

Therefore

$$(3) + (4) \Rightarrow V_1 = V_{cm} + V_d/2 \text{ ---- (5)}$$

$$\text{and } (3) - (4) \Rightarrow V_2 = V_{cm} - V_d/2 \text{ ---- (6)}$$

Substitute eqns (5) & (6) into eqn (2) :

$$V_{OUT} = 1/2[R_3/(R_1+R_3)] [(R_4 + R_2)/R_2 + R_4/R_2]V_d + [R_3/(R_1+R_3)] [(R_4 + R_2)/R_2 - R_4/R_2]V_{cm} \text{ ----- (7)}$$

From this expression, we can find the gain of the differential amplifier

$$\text{Gain} = V_{OUT}/(V_1-V_2)$$

$$= V_{OUT}/V_d$$

$$= 1/2[R_3/(R_1+R_3)] [(R_4 + R_2)/R_2 + R_4/R_2]$$

This gain is known as the **Differential Gain**( $A_d$ ) as it is based on the differential input alone, i.e.

$$A_d = 1/2[R_3/(R_1+R_3)] [(R_4 + R_2)/R_2 + R_4/R_2]$$

As there is another component in  $V_{OUT}$  due to the common-mode component  $V_{cm}$  of the input, we define another gain for the differential amplifier, the **Common Mode Gain** ( $A_{cm}=V_{OUT}/V_{cm}$ ). From eqn (7), this is

$$A_{cm} = [R_3/(R_1+R_3)] [(R_4 + R_2)/R_2 - R_4/R_2]$$

So although a differential amplifier is supposed to amplify the differential component of the input signals, the common component of the input signals (which is the average value of the two input voltages) will also appear at the output. In practice, this common mode component will cause an error in the measurement of the signals.

To eliminate the effect of the common mode component, we can either

(i) make the input common mode component equal to zero, i.e. make  $V_2 = -V_1$  such that the average value of the two input signals equal to zero  
or

(ii) choose the resistor values of  $R_1$  to  $R_4$  in such a way that  $A_{cm}$  is zero.

(i) is usually not possible in practice due to the constraint of the measuring circuitry used to produce  $V_1$  and  $V_2$  (e.g. the Bridge circuit).

(ii) can be achieved theoretically by making  $R_1 = R_2$  and  $R_3 = R_4$ . However, this is not feasible in practice due to the tolerance of the resistors used.


Because of this imperfection, a figure of merit used to describe differential amplifier is the **Common Mode Rejection Ratio (CMRR)**, which is defined as

$$CMRR = 20 \log (A_d/A_{cm})$$

For a perfect differential amplifier, the CMRR is equal to  $\infty$ , as  $A_{cm}$  is zero.

In practice, a CMRR in excess of 80dB to 100dB will be needed for high accuracy measuring system (e.g. a microcomputer data acquisition system). This is very difficult to achieve if the differential amplifier uses discrete resistors for  $R_1$  to  $R_4$ .

## Output:

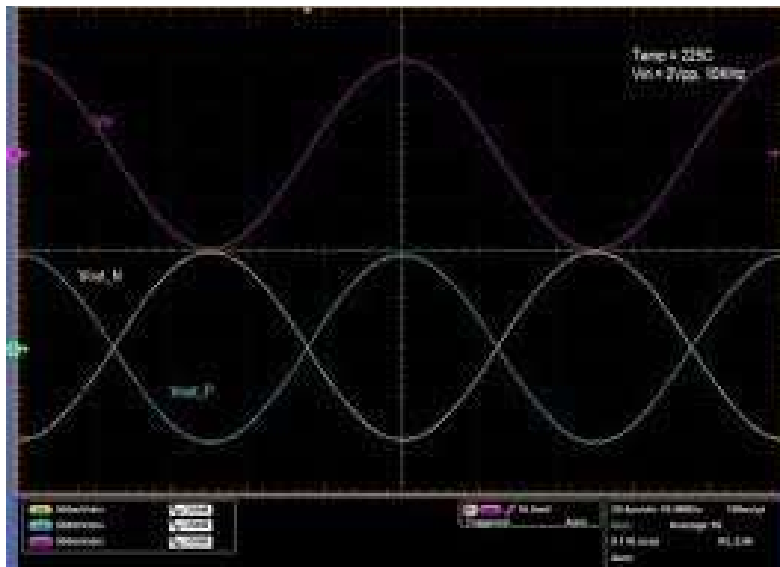

Gain

-----XXXXXXXXXXXXXXXX-----