
 


# CIRCUIT DIAGRAM

---

 

CMOS Inverter

## Theory:

### Inverter Static Characteristics (VTC)

Digital inverter quality is often measured using the Voltage Transfer Curve (VTC), which is a plot of input vs. output voltage. From such a graph, device parameters including noise tolerance, gain, and operating logic-levels can be obtained.

 


Fig.2: Voltage Transfer Curve for a typical 20  $\mu\text{m}$  Inverter

Ideally, the voltage transfer curve (VTC) appears as an inverted step-function - this would indicate precise switching between on and off - but in real devices, a gradual transition region exists. The VTC indicates that for low input voltage, the circuit outputs high voltage; for high input, the output tapers off towards 0 volts. The slope of this transition region is a measure of quality - steep (close to -Infinity) slopes yield precise switching. The tolerance to noise can be measured by comparing the minimum input to the maximum output for each region of operation (on / off). This is more explicitly shown in the fig.3.

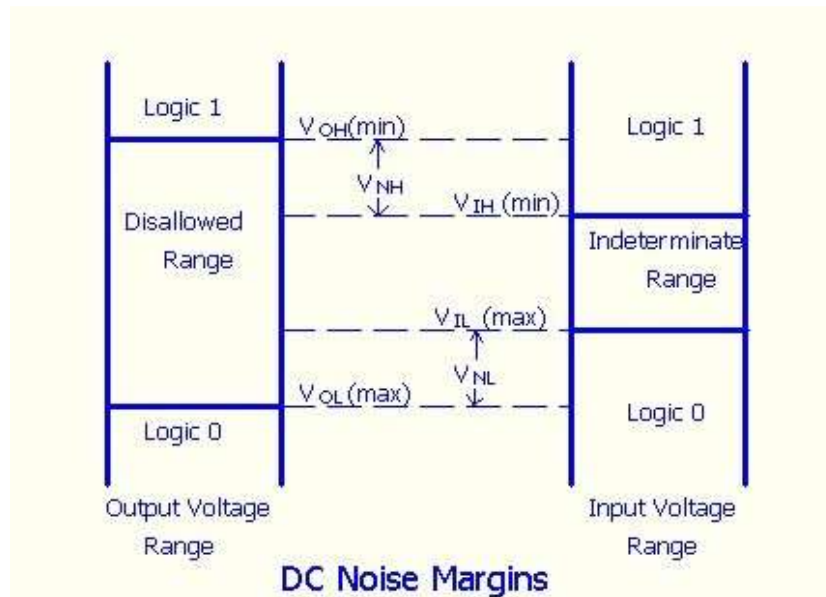


Fig.3: Definition of noise margin

Noise margin : is a parameter intimately related to the transfer characteristics. It allows one to estimate the allowable noise voltage on the input of a gate so that the output will not be affected. Noise margin (also called noise immunity) is specified in terms of two parameters - the low noise margin  $N_L$ , and the high noise margin  $N_H$ . Referring to above figure,  $N_L$  is defined as the difference in magnitude between the maximum LOW input voltage recognized by the driven gate and the maximum LOW output voltage of the driving gate. That is,  $N_L = |$

$V_{IL} - V_{OL}$ . Similarly, the value of  $NH$  is the difference in magnitude between the minimum HIGH output voltage of the driving gate and the minimum HIGH input voltage recognizable by the driven gate. That is,  $NMH = |V_{OH} - V_{IH}|$ . Where  $V_{IH}$ : minimum HIGH input voltage,  $V_{IL}$ : maximum LOW input voltage,  $V_{OH}$ : minimum HIGH output voltage,  $V_{OL}$ : maximum LOW output voltage.

## Inverter Dynamic Characteristics

Fig.4 shows the dynamic characteristics of a CMOS inverter. The following are some formal definitions of temporal parameters of digital circuits. All percentages are of the steady state values.

 


Fig.4: Dynamic characteristics of CMOS inverter

Rise Time ( $t_r$ ) : Time taken to rise from 10% to 90%.

Fall Time ( $t_f$ ): Time taken to fall from 90% to 10%.

Edge Rate ( $trf$ ):  $(t_r + t_f)/2$ .


High-to-Low propagation delay ( $t_{pHL}$ ): Time taken to fall from  $V_{OH}$  to 50%.

Low-to-High propagation delay ( $t_{pLH}$ ): Time taken to rise from 50% to  $V_{OL}$ .

Propagation Delay ( $t_p$ ):  $(t_{pHL} + t_{pLH})/2$ .

Contamination Delay ( $t_{cd}$ ): Minimum time from the input crossing 50% to the output crossing 50%

# Output:

 

## Characteristics of Inverter

XXXXXXXXXXXXXXXXXX